



Figure 1 This circuit adds foldback to a linear regulator.