

$$I_{CQ1} = I_{CQ2} = \frac{V_{CC} - (V_{BE} + 0.7)}{R_Q} = 1.93 \text{ mA}$$

$$I_{CQ3} = I_{CQ4} = \frac{I_{CQ2}}{2} = 0.965 \text{ mA}$$

$$g_{m1} = g_{m2} = (1.93 \text{ mA})(40 \text{ V}^{-1}) = 77.2 \text{ mA/V}$$


$$g_{m3} = g_{m4} = (0.965 \text{ mA})(40 \text{ V}^{-1}) = 38.6 \text{ mA/V}$$

$$r_{\pi 3} = r_{\pi 4} = \frac{\beta}{g_{m3}} = 12590 \Omega$$

$$r_{o3} = r_{o4} = \frac{V_A}{I_{CQ3}} = \frac{100 \text{ V}}{0.965 \text{ mA}} = 103626 \Omega$$

$$r_{TAIL} = \frac{100}{1.93 \text{ mA}} = 51813 \Omega$$

Differential Mode Gain

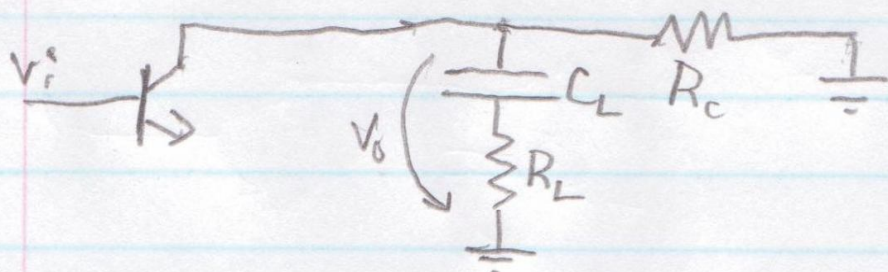

$$\frac{v_o}{v_i} = -g_{mBDT} (R_c \parallel (C_L + R_L))$$

$$= -g_{mBDT} \frac{R_c C_L + R_c R_L}{R_c + C_L + R_L} = \frac{R_c \left(\frac{1}{j\omega C_L} + R_L \right)}{R_c + \frac{1}{j\omega C_L} + R_L}$$

$$= -g_{mBDT} \frac{R_c + j\omega C_L R_L}{j\omega R_c C_L + j\omega R_L C_L + 1}$$