

The Blackboard window for this homework will close at 9:00 am on Monday March 23

For the circuit of Figure 1 below the following component values are given:

$C_a = 10\mu\text{F}$	$R_d = 33\Omega$	$L_c = 47\text{mH}$	$f = 60\text{Hz}$
$R_b = 13\Omega$	$R_c = 12\Omega$	$C_c = 25\mu\text{F}$	
$R_i = 87\Omega$	$L_i = 30\text{mH}$	$M = 19\text{mH}$	

The supply voltage labeled V_s is given by $v_s(t) = 12.\cos(\omega t + \pi/4)$ {Note the phase}

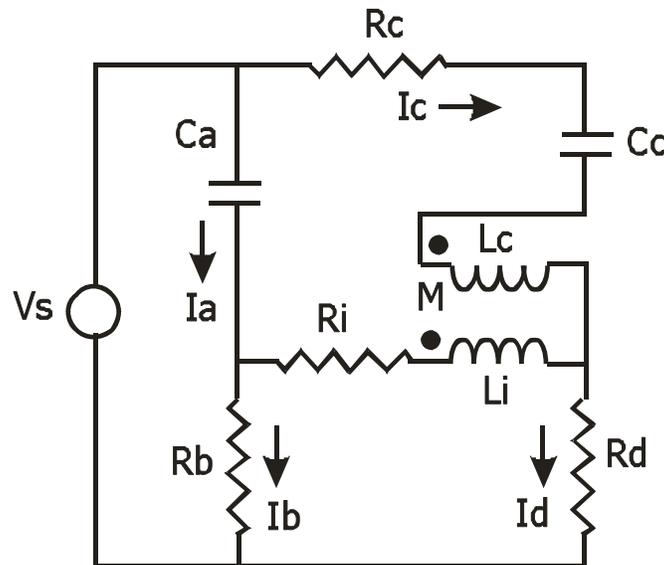


Figure 1

- (1) Determine the amplitude of the current I_a in mA
- (2) Determine the phase of the current I_a in degrees
- (3) Determine the amplitude of the current I_b in mA
- (4) Determine the phase of the current I_b in degrees
- (5) Determine the amplitude of the current I_c in mA
- (6) Determine the phase of the current I_c in degrees
- (7) Determine the amplitude of the current I_d in mA
- (8) Determine the phase of the current I_d in degrees
- (9) Determine the value of the coupling coefficient k