



$Z'_c + iZ_c''$ calculation

Measured phase = θ_m

$$|Z_t| = \frac{V1_{rms}}{I_{rms}} = \frac{V1_{rms}}{V2_{rms}/Z_r}$$

$$Z_c'' = |Z_t| \sin(\theta_m)$$

$$Z'_r + Z'_c = |Z_t| \cos(\theta_m), \text{ then}$$

$$Z'_c = |Z_t| \cos(\theta_m) - Z'_r$$

Therefore

$$|Z_c| = (Z'^2_c + Z''^2_c)^{0.5}$$

$$\theta_c = \tan^{-1} Z_c'' / Z_c'$$

