

How works a resonant converter? Part 2

$$U_C = U_B - U_B \cdot \cos(\omega t)$$

$$I_L = I_{\text{peak}} \cdot \sin(\omega t)$$

$$I_{\text{RMS}} = I_{\text{peak}} / \sqrt{2} \text{ (when sinusoidal)}$$

$$I_{\text{peak}} = C \omega 2 U_C = C \omega 4 U_B$$

$$W_C$$

$$= \int_{-T/2}^{T/2} I_L \cdot U_C \, dt = C \int_{-T/2}^{T/2} \omega 4 U_B \sin \omega t U_B (1 - \cos(\omega t)) \, dt$$

$$= C 4 U_B^2 \omega \int_{-T/2}^{T/2} (\sin(\omega t) - \frac{1}{2} \sin(2\omega t)) \, dt$$

$$\rightarrow W_C = C 4 U_B^2 \cdot \frac{1}{2} = 2 C U_B^2 = 2 Q U_B = \frac{1}{2} W_B$$

There is only half of the energy supplied by the battery on the C!

The other half has dissipated as heat!

What to do to reduce this loss?

Since

$$\omega^2 = 1/LC$$

$$\omega = 2\pi f = 2\pi/T$$

$$Z = \sqrt{L/C} = \text{Impedance}$$

$$I = U/Z$$

The system loss on charging the C can be reduced by selecting C very small and L very large at same frequency ω , so that the charging current I for the capacitor and thus the energy stored on the C gets minimal.

re March 4 2009