

[BRAC UNIVERSITY]

[FALL'13]

[PHY-306]

[BASIC ELECTRONICS]

Assignment-II

Due on : 24th October, 2013

Instructor:
M. L. RAHMAN

Author:

SI:

Sec:

Problem 1

(5 marks) Determine the R_{th} and V_{th} at the terminals $a - b$ of the circuit shown in Fig-1.

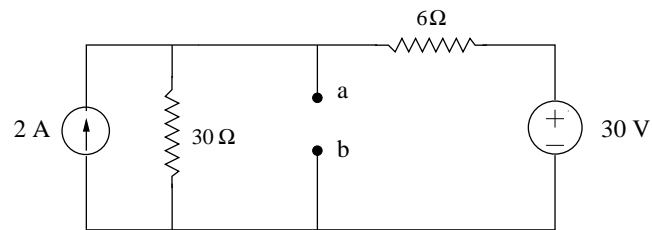


Figure 1: Question-1

Problem 2

(5 marks) Find the Thevenin equivalent circuit looking into the terminals $a - b$ of the circuit shown in Fig-2 and find the value of i_x .

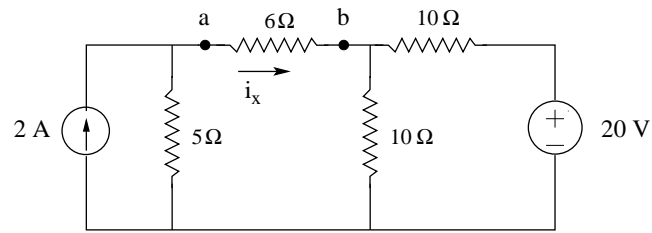


Figure 2: Question-2

Problem 3

(5 marks) Obtain the Norton equivalent circuit of the circuit shown in Fig-3 as viewed from the terminal $a - b$.

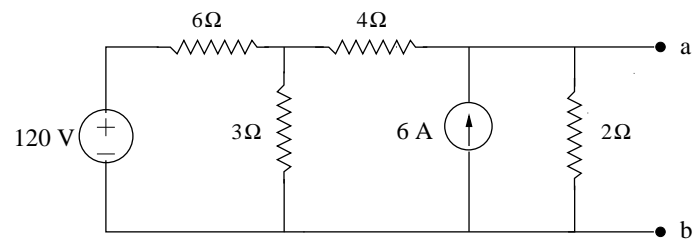


Figure 3: Question-3

Problem 4

(5 marks) Obtain the current through the Galvanometer G , having a resistance of 14Ω , in the Wheatstone bridge shown in Fig-4.

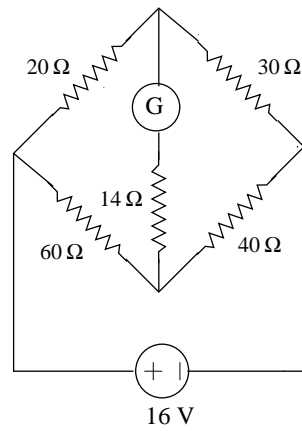


Figure 4: Question-4