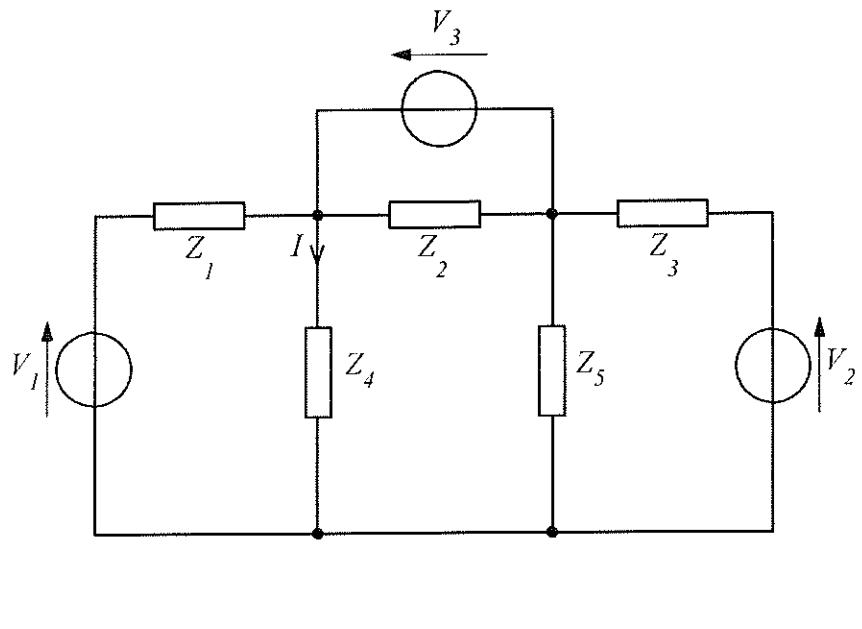



2. Determine, using the values given in TABLE A, the current  $I$  in the circuit of FIGURE 2 by:
- mesh analysis
  - nodal analysis.



$V_1$	$120\angle 0^\circ V$
$V_2$	$120\angle 90^\circ V$
$V_3$	$20\angle 45^\circ V$
$Z_1$	$2 \Omega$
$Z_2$	$-j5 \Omega$
$Z_3$	$4 \Omega$
$Z_4$	$-j5 \Omega$
$Z_5$	$j4 \Omega$

FIG. 2

TABLE A

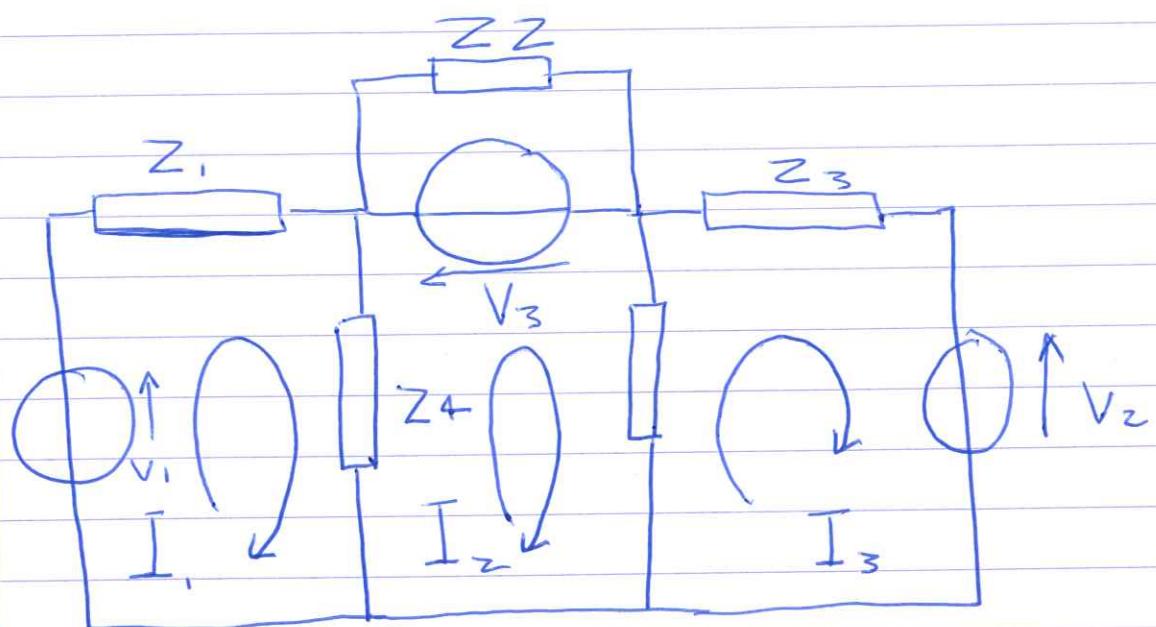

Redrawn circuit

$$V_3 = 14.14 + j14.14$$

loop 1

$$120 - (2)I_1 - (I_1 - I_2)(-j5) = 0$$

loop 2

$$(-j5)(I_2 - I_1) + j4(I_2 - I_3) - 14.14 + j14.14$$

loop 3

$$0 = j4(I_3 - I_2) + 4(I_3) - j120$$

put in form of

$$\text{Volts} =$$

~~120 - 2I<sub>1</sub> - I<sub>2</sub> - I<sub>3</sub>~~

$$120 =$$

$$0 = \text{loop 1} \quad | 120 - (2)I_1 - (I_1 - I_2)(-J5) = 0$$

$$120 = 2I_1 + \cancel{- I_2}, -J5I_1 + J5I_2$$

$$\text{Volts} = 120 = 2 - J5I_1 + J5I_2$$

loop 2

$$0 = (-J5)(I_2 - I_1) + (J4)(I_2 - I_3) - 14.14 + J14.14$$

$$\text{Volts} = 14.14 + J14.14$$

$$14.14 + J14.14 = J5I_1 - J5I_2 + J4I_2 \\ - J4(I_3)$$

$$14.14 + J14.14 = J5I_1 - J1I_2 - J4I_3$$

$$0 = \text{loop 3} \quad \cancel{120} - J4(I_3 - I_2) + 4(I_3) - J120$$

$$\text{Volts} = 120 = J4I_3 - J4I_2 + 4I_3$$

$$\text{so } J120 = (4 + J4)I_3 - J4I_2$$