

Find the  $z$ -parameters of the two-port network given in FIGURE 1.

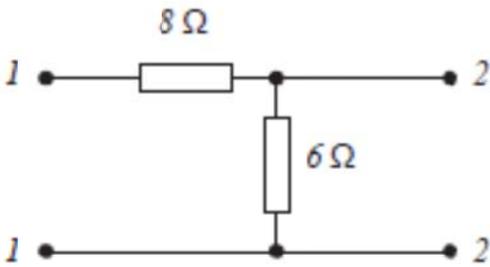


FIG. 1