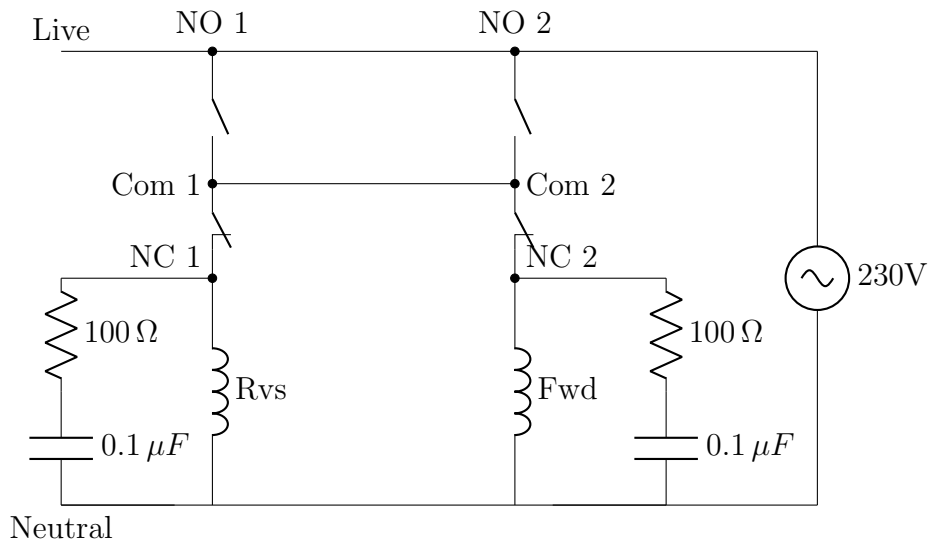


Electrical Interlock Control Circuit

Chat GPT

Thursday 15th May, 2025



Operation Summary

Relay Contact Behavior

- When **Relay 1** is energized:
 - NO 1 closes (connects to Com 1).
 - NC 1 opens (disconnects from Com 1).
- When **Relay 2** is energized:
 - NO 2 closes (connects to Com 2).
 - NC 2 opens (disconnects from Com 2).

When Relay 1 is ON

- Current path:
Live → NO 1 → Com 1 → Com 2 → NC 2 → Fwd coil → Neutral
- **Forward motor is energized.**
- If Relay 2 turns ON, NC 2 opens, disabling the forward motor.

When Relay 2 is ON

- Current path:
Live → NO 2 → Com 2 → Com 1 → NC 1 → Rvs coil → Neutral
- **Reverse motor is energized.**
- If Relay 1 turns ON, NC 1 opens, disabling the reverse motor.

Electrical Interlock

- Prevents both relays from energizing their respective coils simultaneously.
- Cross-wired NC contacts ensure mutual exclusion between forward and reverse drive circuits.

Snubber Protection Considerations

- Each contactor coil is an inductive load and can generate voltage spikes when de-energized.
- A snubber circuit, consisting of a resistor and capacitor in series, is placed across each coil to suppress these spikes.
- This protection reduces arcing at relay contacts, prevents EMI, and prolongs the life of both the coil and control components.
- Recommended values:
 - Capacitor: $0.1 \mu\text{F}$, X2-rated, at least 275VAC.
 - Resistor: 100Ω , rated 1W or higher.
- The RC snubber is connected directly across the terminals of the contactor coil.