
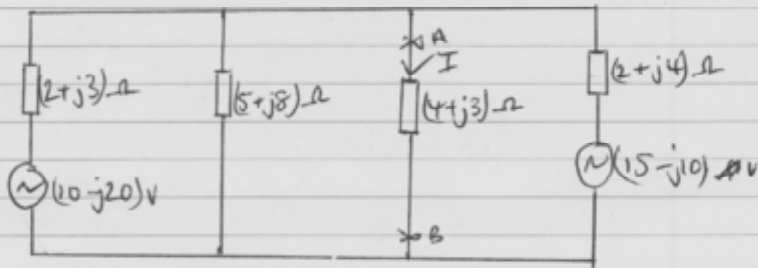


Electrical principles

2.

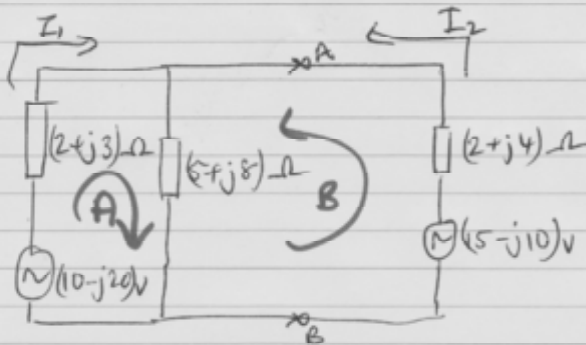

Removing AB and calculating V_{AB}



$$A. (10-j20) - I_1(2+j3) - (5+j8)(I_1+I_2)$$

$$\therefore (10-j20) = (7+j11)I_1 + (5+j8)I_2 \dots ①$$

$$B. (15-j10) - (2+j4)I_2 - (5+j8)(I_1+I_2) = 0$$

$$(15-j10) = (7+j12)I_2 + (5+j8)I_1 \dots ②$$

$$\frac{(10-j20)}{(7-j11)} = I_1 + \frac{(5+j8)}{(7+j11)} I_2 \dots (1)$$

$$\frac{(15-j10)}{(5+j8)} = \frac{(7+j12)}{(5+j8)} I_2 + I_1 \dots (2)$$

$$(1)-(2) \left[\frac{(10-j20)}{(7-j11)} - \frac{(15-j10)}{(5+j8)} \right] = \left[\frac{(5+j8)}{(7+j11)} - \frac{(7+j12)}{(5+j8)} \right] I_2$$

$$(1)-(2) \therefore \left[\frac{22.4 \angle 296.6^\circ}{13 \angle 302.5^\circ} - \frac{18 \angle 326.3^\circ}{9.4 \angle 58^\circ} \right] = \left[\frac{9.4 \angle 58^\circ}{13 \angle 57.5^\circ} - \frac{13.9 \angle 42.5^\circ}{9.4 \angle 58^\circ} \right] I_2$$

$$\therefore [(1.72 \angle -5.9^\circ) - (1.91 \angle 268.3^\circ)] = [(0.723 \angle 0.5^\circ) - (1.48 \angle 15.5^\circ)] I_2$$

$$\therefore [(1.71-j0.177) - (-0.057-j0.91)] = [(0.72 + 0.004j) - (-1.43-j0.4)] I_2$$

$$\therefore (1.227 + j0.12) = (2.153 + j0.406) I_2$$

$$\therefore I_2 = \frac{(1.227 - j0.12)}{(2.153 + j0.406)}$$

$$\therefore I_2 = \frac{1.23 \angle -5.59^\circ}{2.190 \angle 10.7^\circ} = 0.56 \angle -16.29^\circ \text{ Amps}$$

Calculate V_A

$$(15 - j10) - (2 + j4)I_2 = V_A$$

$$\therefore (15 - j10) - (2 + j4)(0.56 \angle -16.29)$$


$$\therefore (15 - j10) - (4.5 \angle 63.4) (\cancel{0.56} 0.56 \angle -16.29)$$

$$\therefore (15 - j10) - (2.03 \angle 47.1)$$


$$\therefore (15 - j10) - (1.38 + j1.49)$$

$$\therefore (13.62 - j8.51) = V_A$$

Short circuit

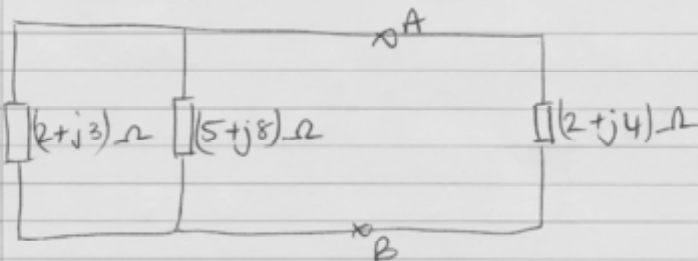

Simplified

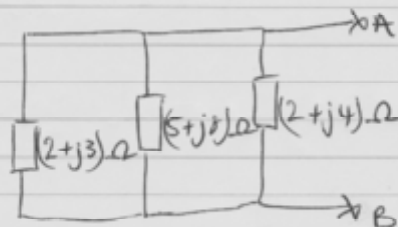

All resistances are parallel

$$\frac{1}{R_{AB}} = \frac{1}{2+j4} + \frac{1}{5+j8} + \frac{1}{2+3j}$$

$$\therefore \frac{1}{R_{AB}} = \frac{1 \angle 0^\circ}{4.47 \angle 63.4^\circ} + \frac{1 \angle 0^\circ}{9.43 \angle 58^\circ} + \frac{1 \angle 0^\circ}{3.6 \angle 56.3^\circ}$$

$$\therefore \frac{1}{R_{AB}} = (0.223 \angle -63.4^\circ) + (0.106 \angle -58^\circ) + (0.278 \angle -56.3^\circ)$$


$$\therefore \frac{1}{R_{AB}} = (0.01 - j1.99) + (0.056 - j0.09) + (0.154 - j0.231)$$

$$\therefore \frac{1}{R_{AB}} = (0.22 - j2.31)$$


$$\therefore R_{AB} = \frac{1}{0.22 - j2.31} = \frac{1 \angle 0^\circ}{2.32 \angle -275.4^\circ}$$

$$0.431 \angle -275.4^\circ = 0.0376 + j0.429$$

$$R_{AB} = (0.38 + j0.43) \Omega$$

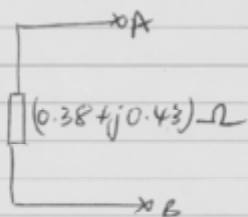

Equivalent thevenin circuit

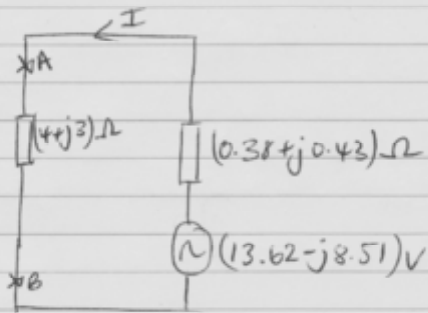

Solving I for equiv circuit;

$$\text{as } (13.62 - j8.51) - (0.38 + j0.43)I - (4 + j3)I = 0$$

$$(13.62 - j8.51) = (-3.62 - j2.57)I$$

$$\frac{(13.62 - j8.51)}{(-3.62 - j2.57)} = -I$$

$$\therefore \frac{16.1 \angle -32^\circ}{4.44 \angle 35.4^\circ} = -(3.63 \angle 292.6^\circ) \text{ Amp}$$

$$\therefore -3.63 \angle 67.4^\circ$$

$$\underline{(-1.39 - j3.35) \text{ A}}$$