


*"Pessimism is just an ugly word for pattern recognition."*

*-Anonymous*

**Problem 1 Quickie**

(12.5 points)

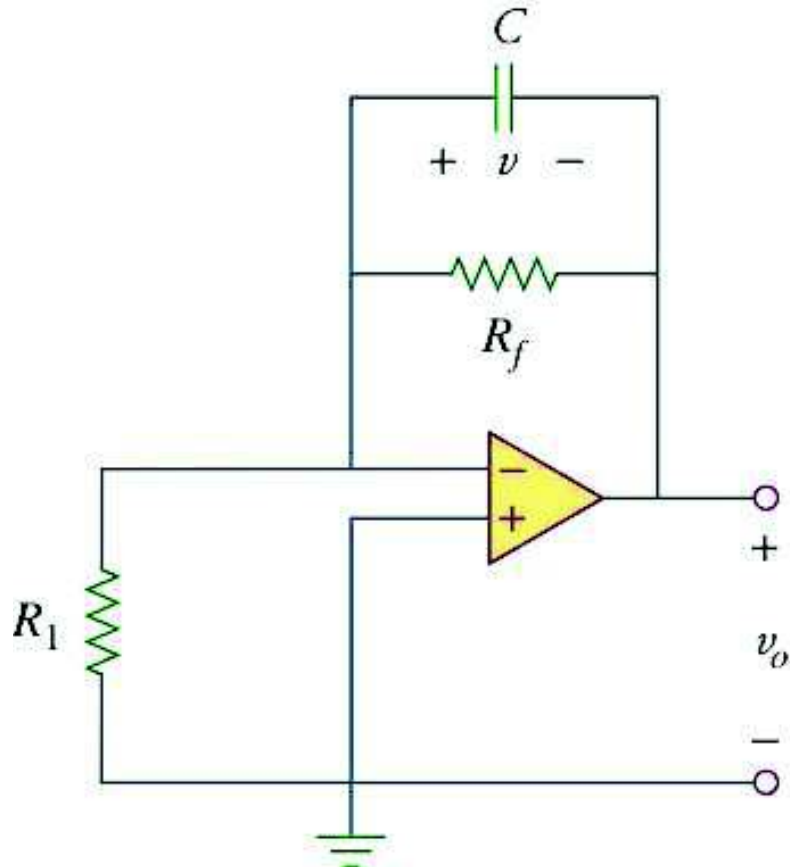a) In the box below, provide a symbolic expression for  $v_o$  for  $t > 0$  if  $v(0) = 4 \text{ V}$ .





b) If  $R_f = 40 \text{ k}\Omega$ ,  $R_1 = 10 \text{ k}\Omega$ ,  $C = 10 \text{ }\mu\text{F}$ , and  $v(0) = 4 \text{ V}$ , write the expression for  $v_o$  for  $t > 0$  in the **BOX BELOW**. *(2.5 points)*


*"If a person offends you... do not resort to extremes,  
simply watch your chance and hit him with a brick."*

- Mark Twain

**Problem 2** First order circuits

(25 points)

Consider the circuit below.

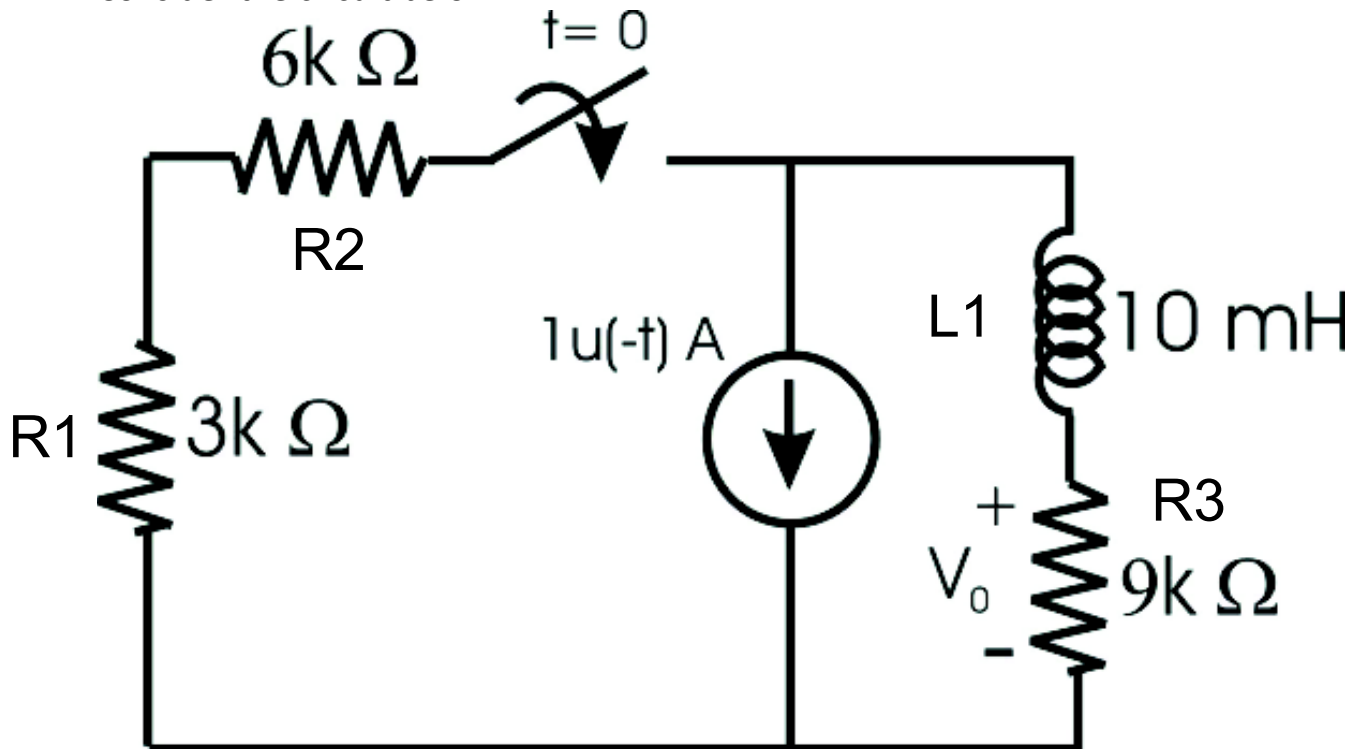

a) What is the value of  $V_0$  at  $t = 0^+$ ? Write It in the BOX BELOW. (5 points)



b) Using whatever method you like (yes, anything, don't raise your hand to ask if you can use **XXX**), provide a **symbolic expression** for the voltage  $V_0(t)$  for  $t > 0$  in the **BOX BELOW**. (17.5 points)

c) Using the values provided in the figure, provide an expression for the voltage  $V_0(t)$  for  $t > 0$  in the **BOX BELOW**. *(2.5 points)*