



$$V = 10V$$

$$C = 10\mu F$$

• charge on  $C_1$  &  $C_2$

$$Q_1 = 10V \cdot 10\mu F = 1.0 \times 10^{-4} C$$

$\downarrow$   
 $.000010F$

$$Q_{C2} = ?$$