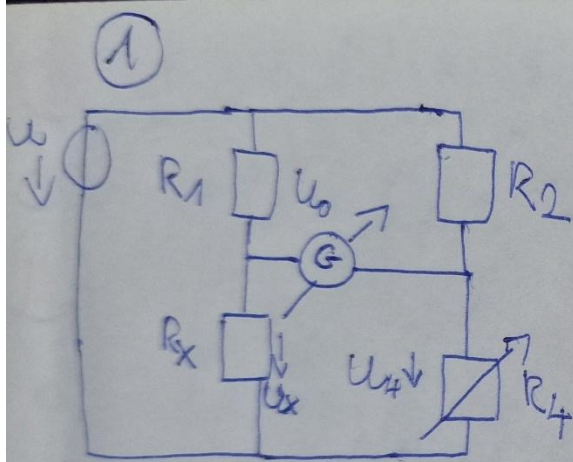


(1)



Balanced bridge

$$U_0 = 0 \Rightarrow U_x - U_4 = 0$$

$$U_x = U_4$$

$$U_0 = U \left(\frac{R_x}{R_1 + R_x} - \frac{R_4}{R_2 + R_4} \right) = 0$$

$$U_x = U \cdot \frac{R_x}{R_1 + R_x}$$

$$U_4 = U \cdot \frac{R_4}{R_2 + R_4}$$

(2)

1. Definition

A **strain gauge** is a sensor that measures **mechanical strain** (deformation) by converting it into an **electrical resistance change**.

2. Mechanical ↔ Electrical Relationship

Mechanical Input: Strain (ϵ) = $\Delta L / L$ (relative length change)

Electrical Output: $\Delta R / R = \text{Gauge Factor (GF)} \times \epsilon$

where:

ΔR = Change in resistance

R = Original resistance

GF = Gauge Factor

3. Working Principle

Piezoresistive Effect: When the gauge is stretched or compressed:

Its **resistive foil/wire** deforms, altering its cross-section and length.

This changes its **electrical resistance** (ΔR).

Wheatstone Bridge Circuit: Used to measure small resistance changes accurately.

4. Applications


Load cells (force measurement)

Structural health monitoring (e.g., bridges, aircraft)

Pressure sensors

Key Formula:
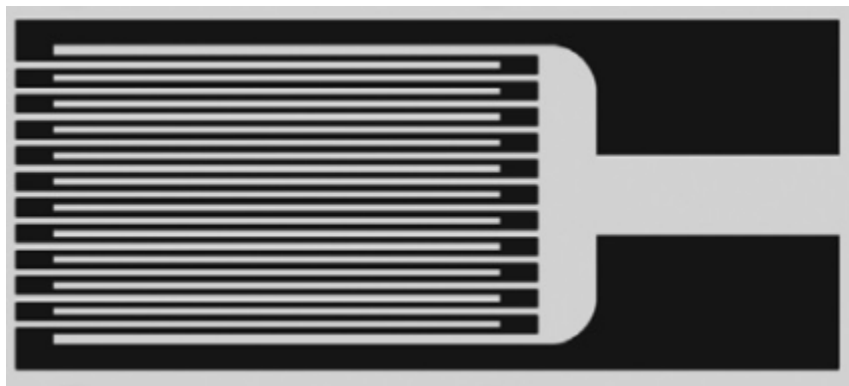
$$\frac{\Delta R}{R} = \text{GF} \cdot \epsilon$$



(3)

$$\textcircled{3} I_n = 3 \text{ A}, U_n = 300 \text{ V}$$

$$\cos \varphi = 1, \text{ scale rate } 150, L_1 = 60^\circ$$

$$L_2 = 72 \quad P_0 = 0,2$$

a) It can be used in a symmetric system without a neutral wire

$$P = P_1 + P_2$$

~~(2.2.1)~~

$$P_n = U_n \cdot I_n \cdot \cos \varphi = 300 \cdot 3 \cdot 1 = 900 \text{ [W]}$$

$$C = \frac{P_n}{I_{\text{max}}} = \frac{900}{150} = 6 \left[\frac{\text{W}}{\circ} \right]$$

$$P_1 = C \cdot L_1 = 6 \frac{\text{W}}{\circ} \cdot 60^\circ = 360 \text{ [W]}$$

$$P_2 = C \cdot L_2 = 6 \frac{\text{W}}{\circ} \cdot 72^\circ = 432 \text{ [W]}$$

$$k_{P1} = \frac{P_1}{P_1 + P_2} = \frac{360}{792} = 0,45 \quad \left. \begin{array}{l} k_{P1} = \frac{P_n}{P_1} \cdot P_0 = \frac{900}{360} \cdot 0,2 = \\ = 0,5 \end{array} \right\} 792 \text{ [W]}$$

$$k_{P2} = \frac{P_2}{P_1 + P_2} = 0,545 \quad \left. \begin{array}{l} k_{P2} = \frac{P_n}{P_2} \cdot P_0 = \frac{900}{432} \cdot 0,2 = \\ = 0,42 \end{array} \right\}$$


$$k_P = \sqrt{(k_{P1} \cdot k_{P1})^2 + (k_{P2} \cdot k_{P2})^2} = \sqrt{(0,45 \cdot 0,5)^2 + (0,545 \cdot 0,42)^2}$$
$$= 0,32\%$$

$$Q = \sqrt{3} (P_2 - P_1) = \sqrt{3} (432 - 360) =$$
$$= 124,7 \text{ [VA]}$$

$$S = \sqrt{P^2 + Q^2} = \sqrt{792^2 + 124,7^2} = 801,76 \text{ [VA]}$$

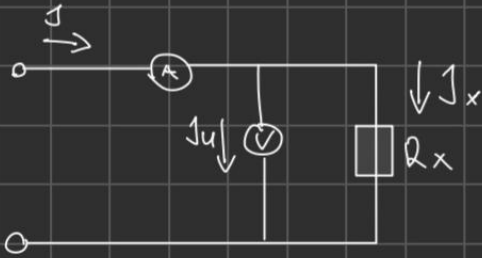(4)

$I = 0,8$; $U = 24$; $R_u = 2000$; $U_{mh} = 50$; $I_{mh} = 1,5$; $k_{po} = 0,5$; $R_j = 0,5$



1. We calculate it in volts (V)

a)

$$I = \frac{U}{R_u} + \frac{U}{R_x}$$

$$0,8 = \frac{24}{2000} + \frac{24}{R_x}$$

$$0,8 = 0,012 + \frac{24}{R_x}$$

$$0,788 = \frac{24}{R_x}$$


$$R_x = \underline{\underline{30,45 \Omega}}$$

b)

$$h = \frac{U_{mh}}{U} \cdot k_{po}$$

$$h = \frac{50V}{24V} \cdot 0,5$$

$$h = \underline{\underline{1,04\%}}$$

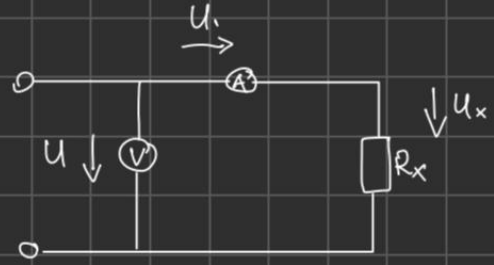

2. We calculate it in ampere (A)

a)

$$R_x = \frac{U}{I} - R_1$$

$$R_x = \frac{24}{0,8} - 0,5$$

$$R_x = \underline{\underline{29,5 \Omega}}$$

b)

$$h = \frac{I_{mh}}{I} \cdot k_{po}$$

$$h = \frac{1,5A}{0,8A} \cdot 0,5$$

$$h = \underline{\underline{0,9375\%}}$$

The ammeter has a smaller measurement error.

(5)

a)
$$h = \frac{U_{mh}}{U_m} \cdot h_{p0} = \frac{10V}{3V} \cdot 0,5 = \underline{\underline{1,66\%}}$$

b)
$$h = \frac{U_{mh}}{U_m} \cdot h_{p0} = \frac{5}{3} \cdot 1,5 = \underline{\underline{2,5\%}}$$

c)
$$U_{mh} = 20V \rightarrow \begin{matrix} 19,99 \\ 19,97 \end{matrix} \left. \vphantom{\begin{matrix} 19,99 \\ 19,97 \end{matrix}} \right\} 2 \text{ digit} = 0,02$$

$$\underline{(19,99 \cdot 0,002) + 0,02} = 0,06$$

0,2% 2D

Deviation

$$x_w = 3 - 0,06 = 2,94V$$

$$H = x_m - x_w = 3 - 2,94 = 0,06$$

$$h = \frac{H}{x_w} = \frac{0,06}{2,94} = 0,02 = \underline{\underline{2\%}}$$

U(measured)

U(measured)

Absolute error

Relative error

(6)

a) Period (T), Phase angle difference or Phase shift, Frequency

b) $\sin \varphi = \frac{X_m}{X} = \frac{4,5}{5} = 0,9 \quad / \sin^{-1}$

$\varphi = \underline{\underline{64,16^\circ}}$

