

Problem 1

Design an RC low pass filter with a cut-off frequency of 8 KHz. You have to use a resistance of 10 kΩ.

$$\omega_c = \frac{1}{RC}$$

$$\omega_c = 2\pi \times 8000 \text{ rad/s}$$

$$R = 10 \times 10^3 \Omega$$

$$\text{So, } C = \frac{1}{R\omega_c} = \frac{1}{10 \times 10^3 \times 2\pi \times 8000}$$

$$= 1.9894 \times 10^{-9} \text{ F} = 1.9894 \text{ nF}$$

Problem 2

Find the Thevenin equivalent circuit with respect to terminal AB



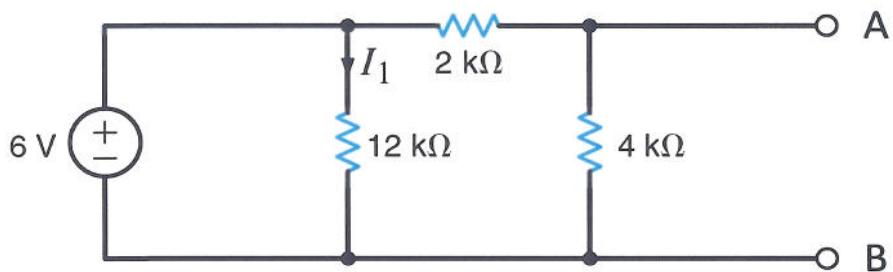


Figure 1: Circuit for problem 2

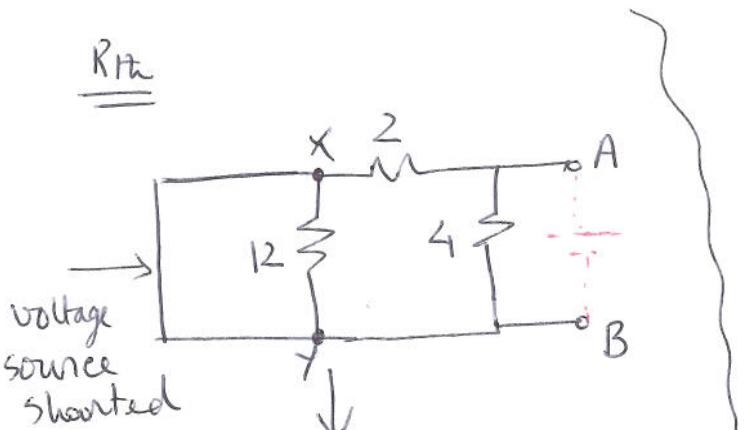


$$2||4 = \frac{2 \times 4}{6} = 1.33 \text{ k}\Omega$$

12kΩ is shorted out
X, Y same point

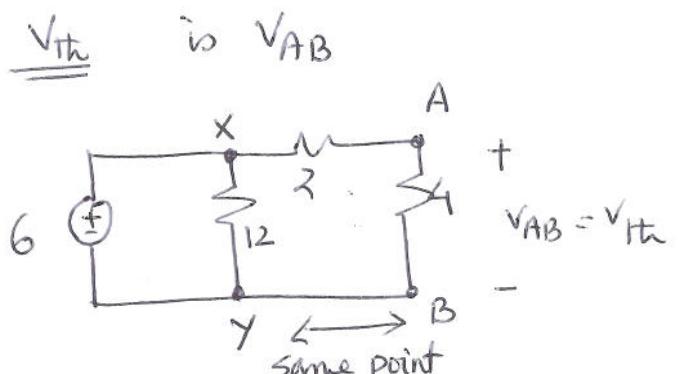

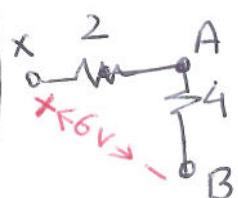$V_{XY} = 6 \text{ V}$ ← 2 kΩ is connected across the source




2 4 k resistances in series.


so apply voltage division.

$$V_{AB} = 6 \times \frac{4}{2+4} = 4 \text{ volt } 4 \text{ } V_{Th}$$

So Thvenin equivalent circuit :

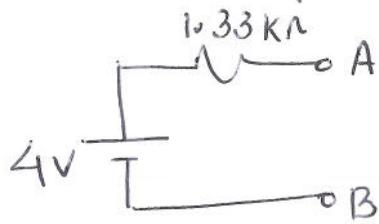

Alternate way of finding V_{Th}

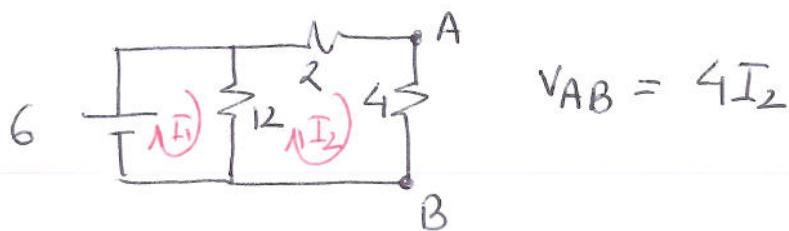

$$12I_1 - 12I_2 = 6 \quad \text{---(1)}$$

$$-12I_1 + 18I_2 = 0 \quad \text{---(2)}$$

$$6I_2 = 6 \Rightarrow I_2 = 1 \text{ mA}$$

$$\text{So } V_{AB} = 4 \times 1 = 4 \text{ volts}$$



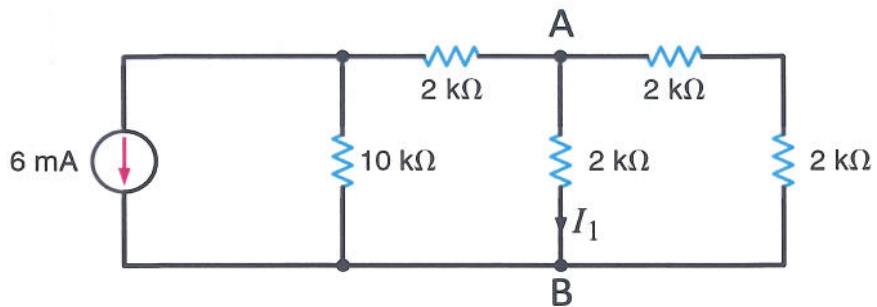
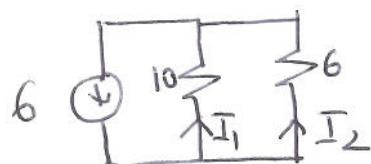
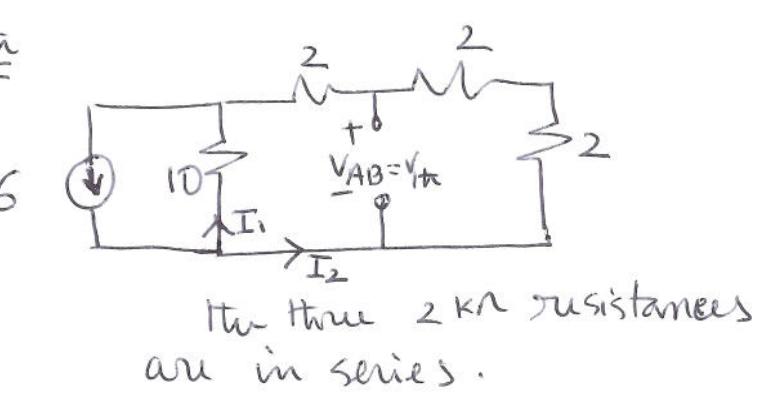
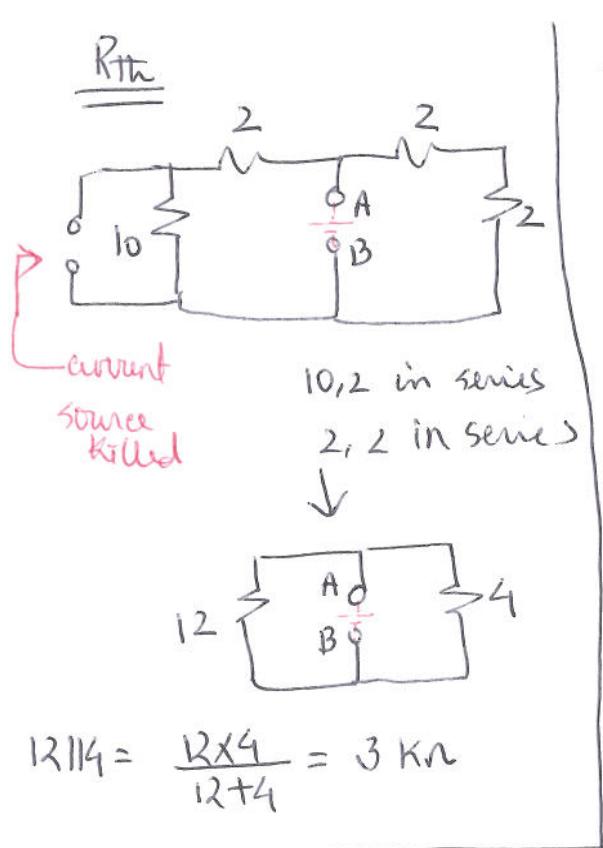


Figure 2 Circuit for problem 2

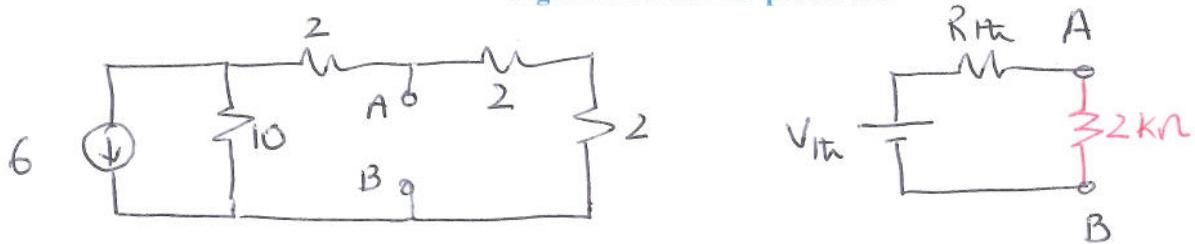


$$I_2 = 6 \times \frac{10}{10+6} \quad \text{current division}$$

$$= 3.75 \text{ mA}$$

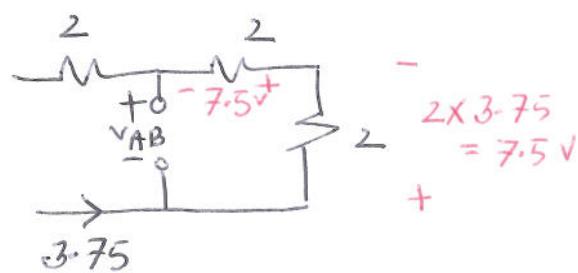

So Thévenin equivalent ckt:

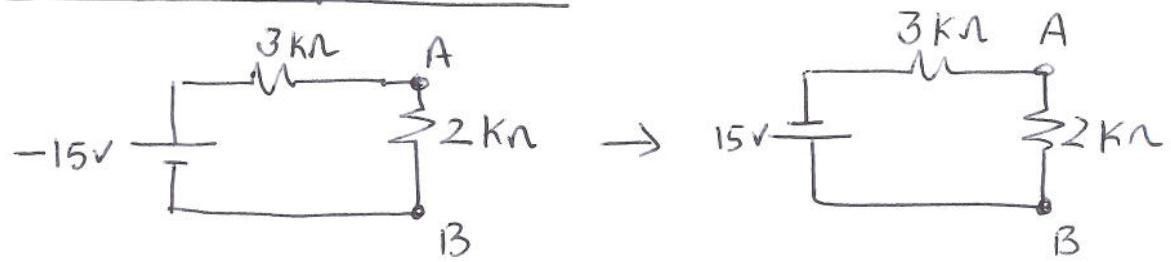



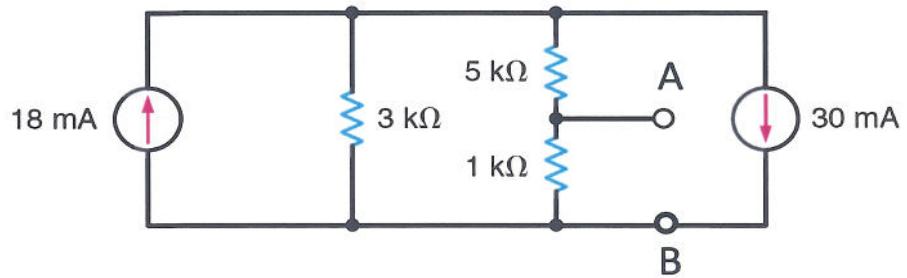


Figure 3 Circuit for problem 2

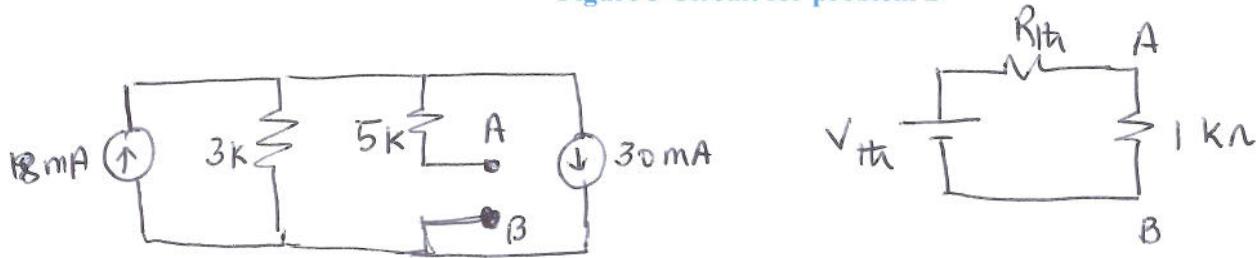



$$\begin{aligned}
 & \underline{R_{th}} \\
 & \text{Circuit diagram: } 18 \text{ mA source up, } 3 \text{ k}\Omega \text{ in series, } 5 \text{ k}\Omega \text{ in parallel with terminals A and B, } 30 \text{ mA source down.} \\
 & R_{th} = 3 + 5 = 8 \text{ k}\Omega \\
 & \underline{V_{th}} \\
 & \text{Circuit diagram: } 18 \text{ mA source up, } 3 \text{ k}\Omega \text{ in series, } 5 \text{ k}\Omega \text{ in parallel with terminals A and B, } 30 \text{ mA source down.} \\
 & V_{AB} = V_{th} \\
 & I = 30 - 18 = 12 \text{ mA}
 \end{aligned}$$

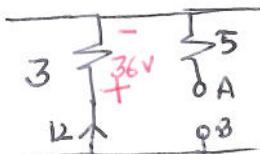$V_{AB} = -36 \text{ V}$
 \rightarrow no drop in the 5 kΩ resistor as no current.





Equivalent ckt

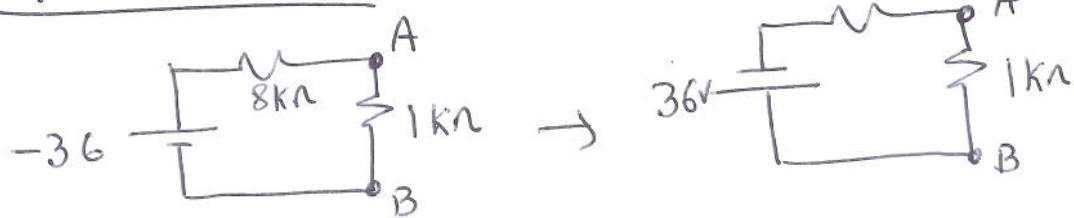

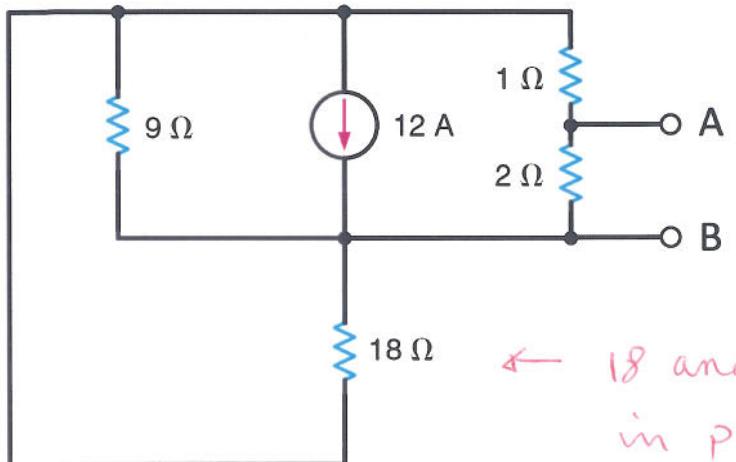

$\leftarrow 18 \text{ and } 9$
in parallel

Figure 4 Circuit for problem 2

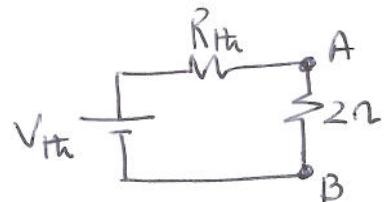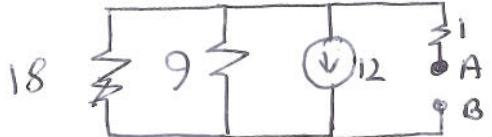

$$\frac{R_{Th}}{18}$$


$$R_{Th} = 6 + 1 = 7 \Omega$$

$$\frac{V_{Th}}{18}$$

\rightarrow current (open)

$$I_1 = 12 \times \frac{18}{9+18} \quad \leftarrow \text{current division}$$


$$= 8 \text{ Amp}$$

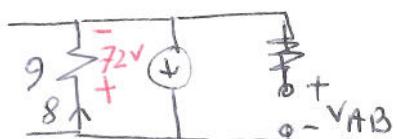

$$V_{AB} = -72 \text{ V} = V_{Th}$$

Equivalent circuit

Equivalent ckt

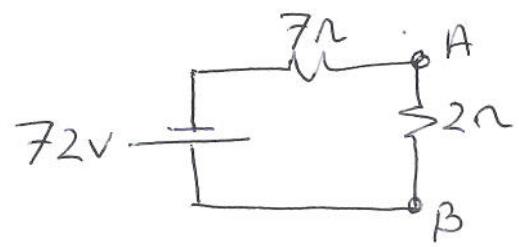


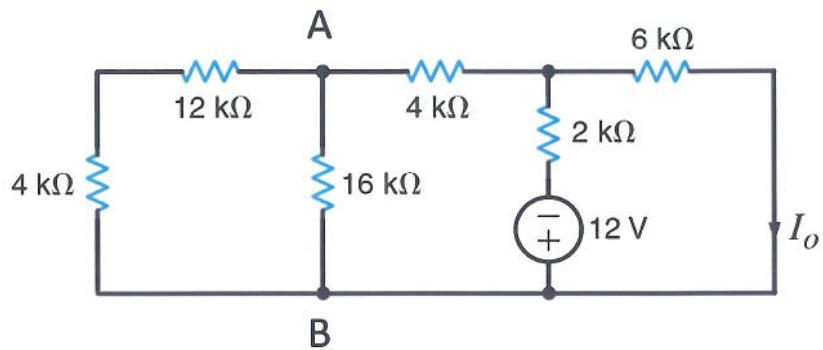
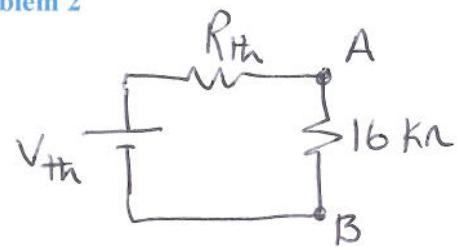


Figure 5 Circuit for problem 2

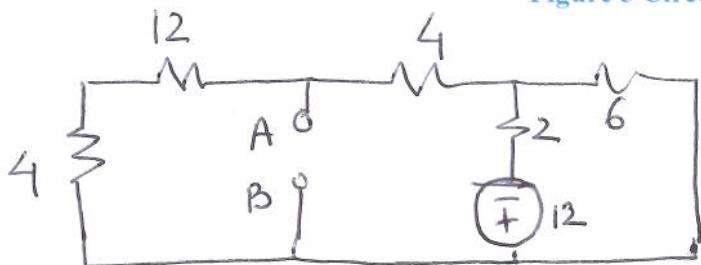


$$\frac{R_{Th}}{16}$$

series \rightarrow 12 \rightarrow 4 *parallel* \rightarrow 6

$\Rightarrow 16 \parallel 5.5 = \frac{6 \times 2}{2+6} = 1.5$

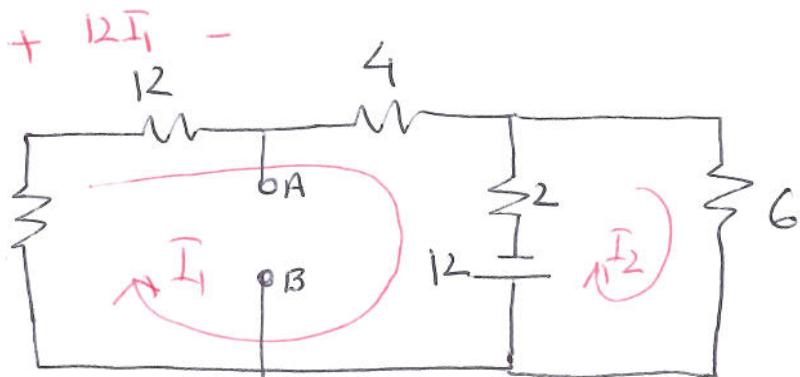$16 \parallel 5.5 \Rightarrow R_{Th} = 16 \parallel 5.5 = \frac{16 \times 5.5}{16 + 5.5} = 4.093 \text{ k}\Omega$



Bolt gains
A \rightarrow B

$$V_{AB} = -12I_1 - 4I_2 \\ = -16I_1$$

$$(4+12+4+2)I_1 - 2I_2 = 12$$

$$\Rightarrow 22I_1 - 2I_2 = 12 \quad \text{--- (1)}$$

$$-2I_1 + 8I_2 = -12 \quad \text{--- (2)}$$

$$\underline{4 \times (1) + (2)}$$


$$88I_1 - 8I_2 = 48$$

$$-2I_1 + 8I_2 = -12$$

$$\underline{86I_1 = 36} \Rightarrow I_1 = \frac{36}{86} \text{ mA} = 0.4186 \text{ mA}$$

$$\therefore V_{AB} = -16I_1 = -6.6977 \text{ volt}$$

Equivalent ckt

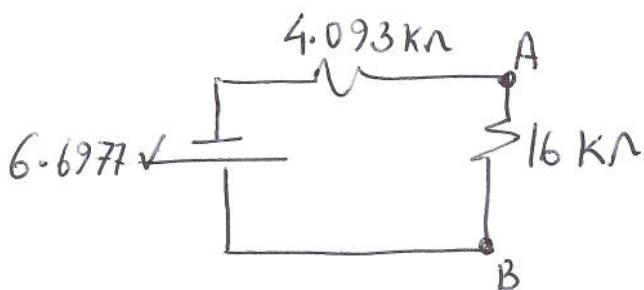



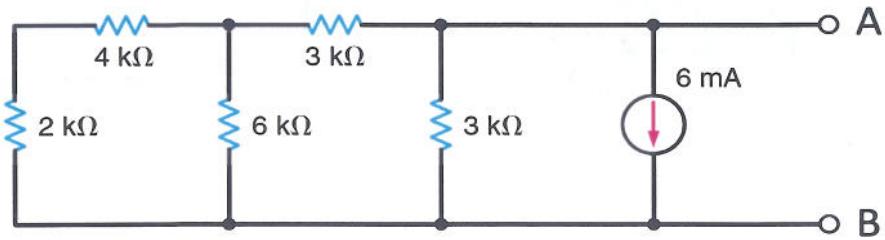


Figure 6 Circuit for problem 2

R_{Th} open current source to kill

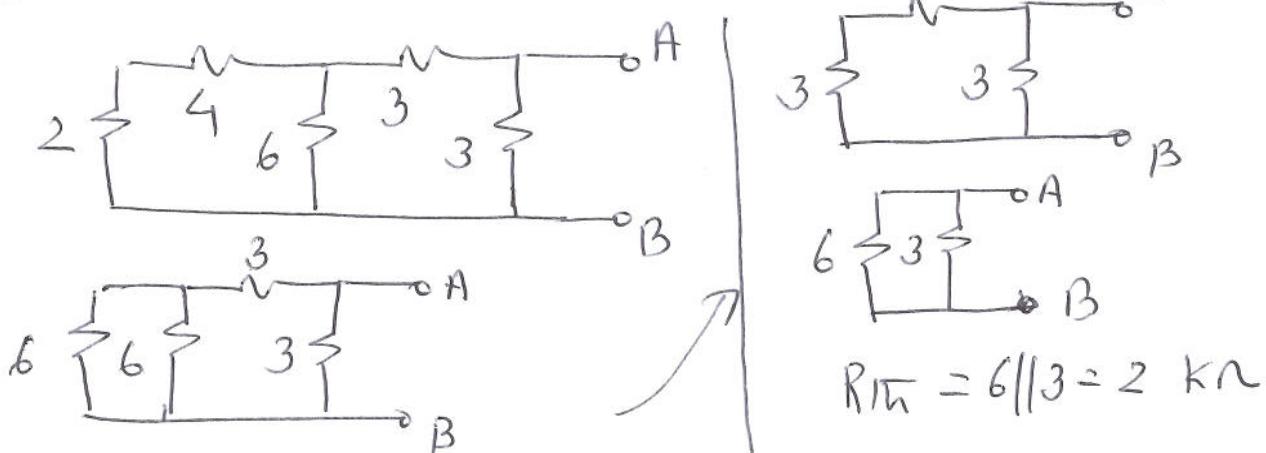



V_{Th}

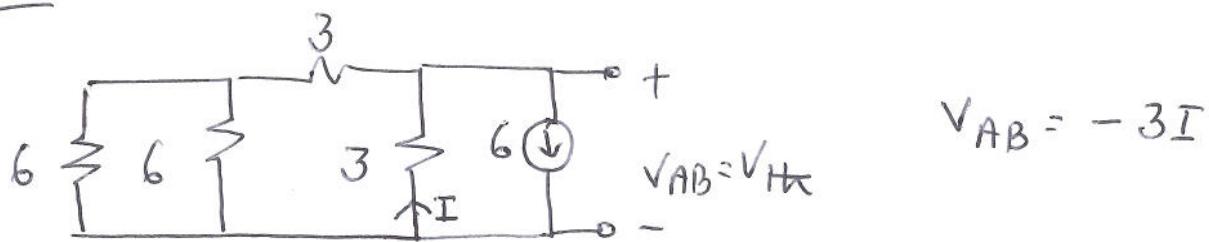

$$I = 6 \times \frac{6}{6+3} = 4 \text{ mA}$$

$$\therefore V_{AB} = V_{Th} = -3I = -12 \text{ V}$$

Equivalent ckt

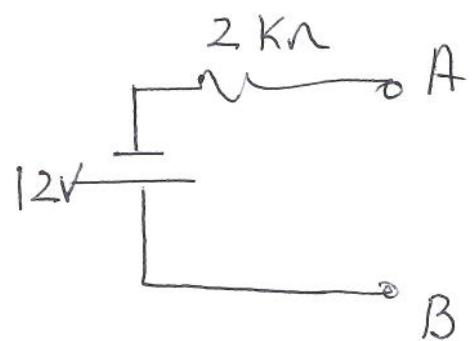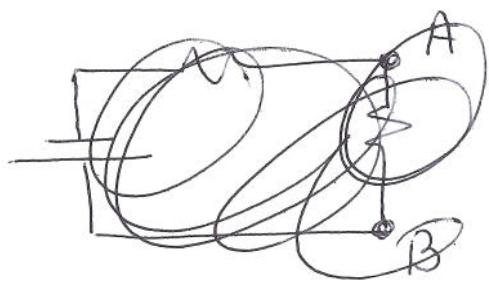



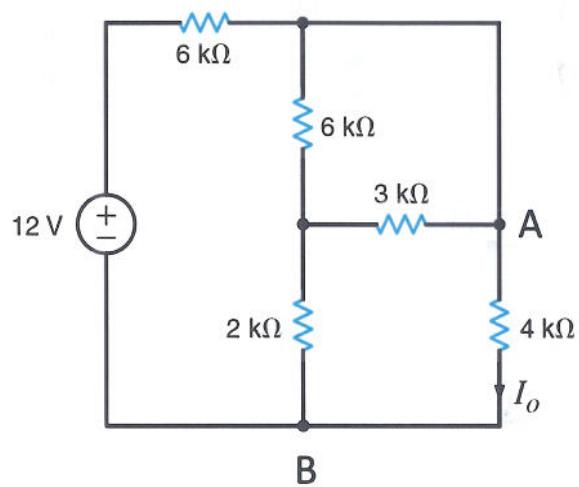
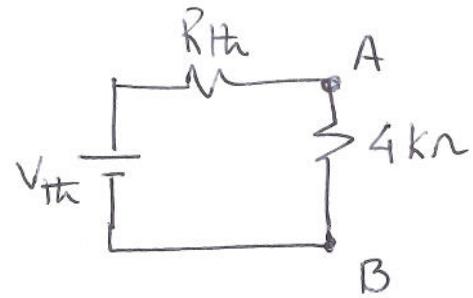
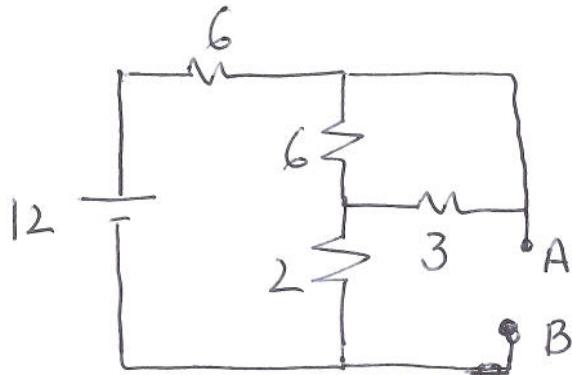




Figure 7 Circuit for problem 2

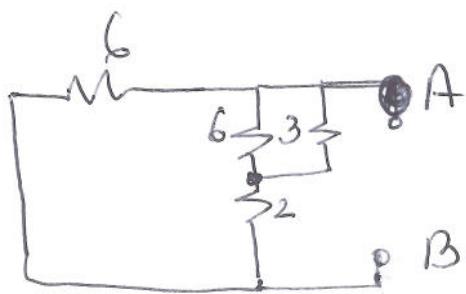

R_{th}



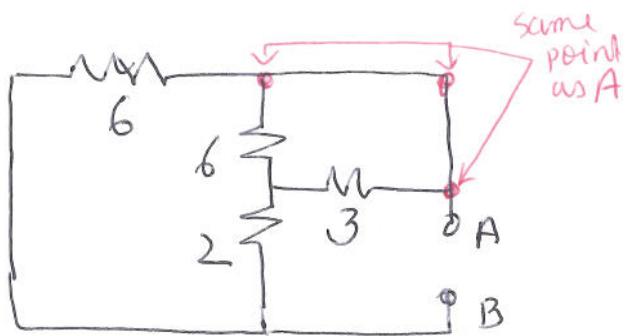


$$6 \parallel 3 = 2$$

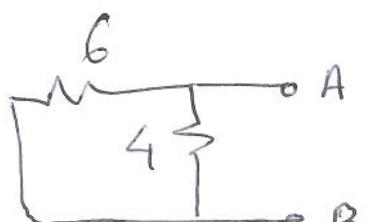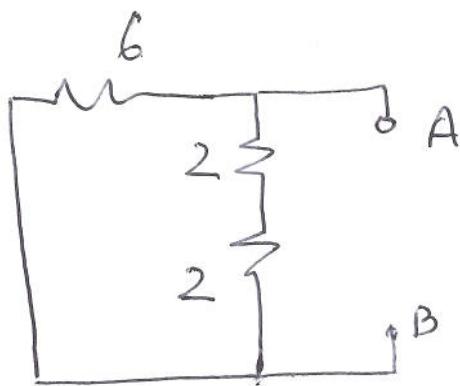

$$R_{th} = 6 \parallel 4 = 2.4 \text{ k}\Omega$$


V_{th}

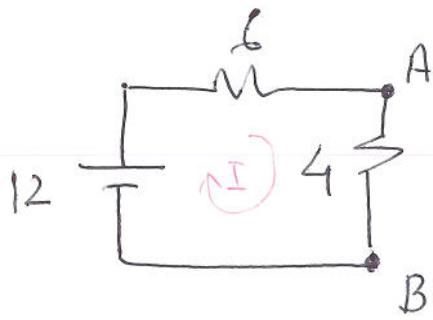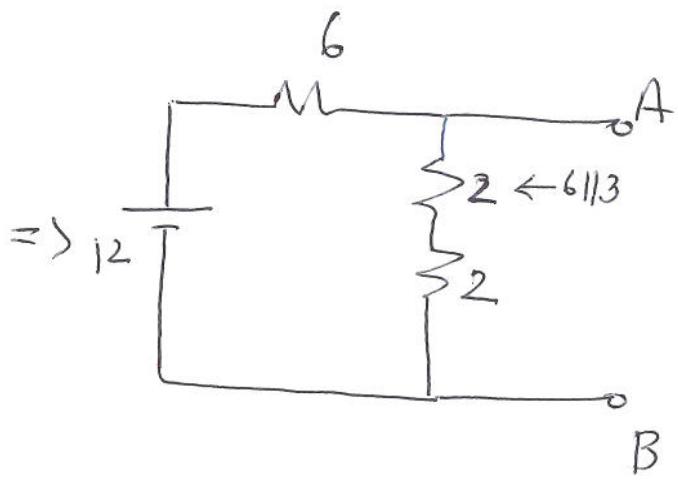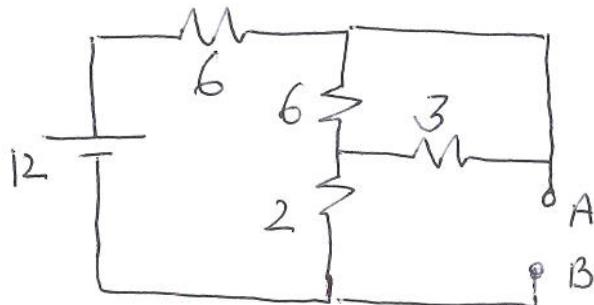


$$V_{AB} = V_{th} = 12 \times \frac{4}{4+6} = 4.8 \text{ V}$$

$$\text{Alternatively } I = \frac{12}{6+4}, \quad V_{AB} = 4I$$

Equivalent CKT

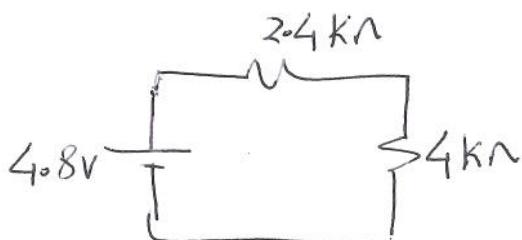

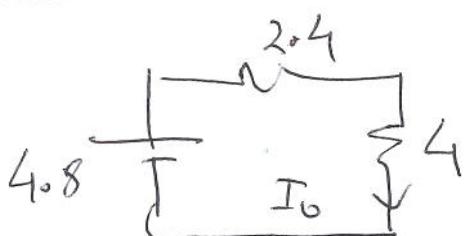* If we wanted to find I_o as shown in the ekt:



$$I_o = \frac{4.8}{6.4} \text{ mA}$$

$$= 0.75 \text{ mA}$$

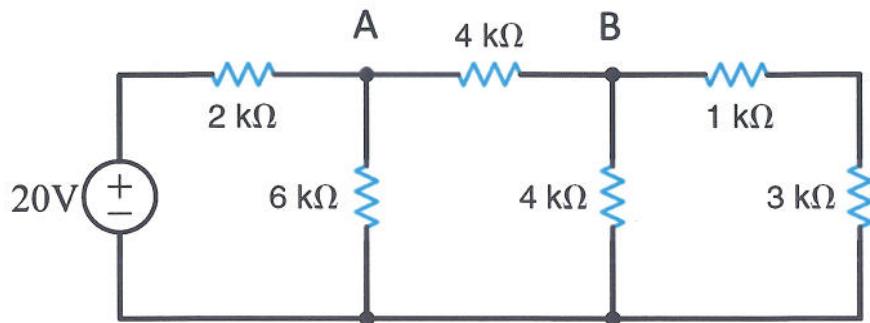


Figure 8 Circuit for problem 2

R_{th}

$$2/6 = \frac{2 \times 6}{2+6} = 1.5$$

$$R_{th} = 2 + 1.5 = 3.5 \text{ k}\Omega$$

V_{AB}

$$I = \frac{12}{8} = 1.5 \text{ mA}$$

$$V_{AB} = 9 + 0 = 9 \text{ V}$$

Equivalent ckt

