

→ kVL is based on Conservation of Charge according to this the algebraic Sum of Current at a node is (zero).

→ Applying KCL at Point B

$$\frac{V_b - V_a}{10} + \frac{V_b}{2} + \frac{V_b}{100k} = 0$$

Taking approximation ($\frac{V_b}{100k} \ll \frac{V_b}{2}$)

$$V_b - 12 + 5V_b = 0$$

$$\frac{6V_b}{8} = \frac{12}{6}$$

$$\therefore V_b = 2V$$

$$\rightarrow \text{So, } I_1 = \frac{12 - 2}{10} = 1A$$

$$\Rightarrow I_3 = \frac{2}{100k} = 2 \times 10^{-5} A \quad (\text{Ideal diode})$$

$$\Rightarrow I_3 = \frac{2 - 0.7}{100k} = 1.3 \times 10^{-5} A \quad (\text{For Silicon diode})$$

$$\Rightarrow I_2 = \frac{2}{2} - 2 \times 10^{-5} \approx 1A$$

→ In Second approximation the diode is Considered as Forward biased diode with battery to turn on the device, now according to the question each independent source by 10% .

$$\text{So, } V_a = 12 + \frac{1}{10} \times 12 = 13.2V$$

$$\Rightarrow R_1 = 10 + 1 = 11\Omega$$

$$\Rightarrow R_2 = 2 + 0.2 = 2.2\Omega$$

$$\Rightarrow R_3 = 100k + 10k = 110k\Omega$$

or V_b applying KCL

$$\frac{V_b - V_s}{11} + \frac{V_b}{2.2} + \frac{V_b}{100K} = 0$$

(Tulcing approximation) $\frac{V_b}{100K} \ll \frac{V_b}{2}$

$$\therefore \frac{V_b}{11} - \frac{13.2}{12} + \frac{V_b}{2.2} = 0$$

$$= \frac{V_b}{11} + \frac{V_b}{2.2} - \frac{13.2}{12} = 0$$

$$= 0.545 V_b - 1.1 = 0$$

$$V_b = \frac{1.1}{0.545}$$

$$\therefore V_b = 2.02 V$$

So,

$$V_s = V_a = 13.2 V$$

$$V_b = 2.02 V$$

$$V_c = 2.02 V \rightarrow (\text{if diode is ideal})$$

$$V_c = (2.02 - 0.7) = 1.32 \rightarrow (\text{if it is silicon diode})$$

→ The barrier potential of silicon diode is

$$\Rightarrow I_1 = \frac{V_a - V_b}{11} = \frac{13.2 - 2.02}{11} = 1.01636 A$$

$$\Rightarrow I_3 = \frac{2.02}{100K} = 2.02 \times 10^{-5} A \rightarrow (\text{For ideal diode})$$

$$\Rightarrow I_3 = \frac{2.02}{2} = 1.01 A \quad I_3 = 1.3 \times 10^{-5} \text{ (For silicon)}$$

→ we know power equation $P = I^2 \times R$

$$\therefore P_1 = (1.01636)^2 \times 13.2 = 13.635 W$$

$$P_2 = (1.01)^2 \times 2 = 2.0402 W$$

$$P_3 = (2.02 \times 10^{-5})^2 \times (10 \times 10^3) = 4.48 \times 10^{-5} W$$

$$V_s = 12$$

