
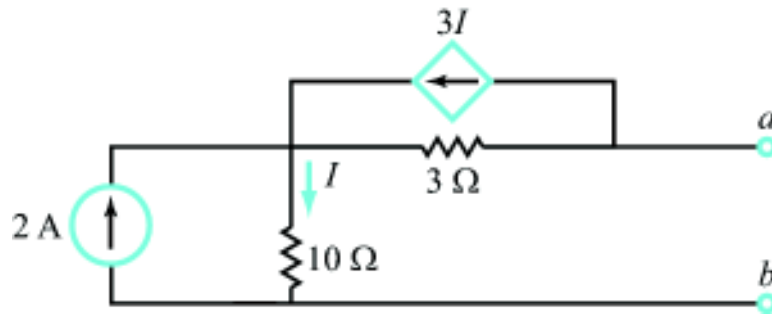


**Exercise 3-13** Find the Norton equivalent at terminals  $(a, b)$  of the circuit in Fig. E3-13.

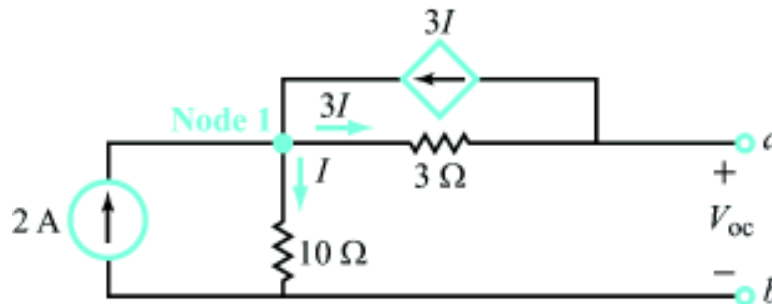

**Figure E3-13**

**Solution:** Thévenin voltage




At node 1:

$$I = 2 \text{ A.}$$

Hence,

$$V_{Th} = V_{oc} = 10I - 3 \times 3I = I = 2 \text{ V.}$$

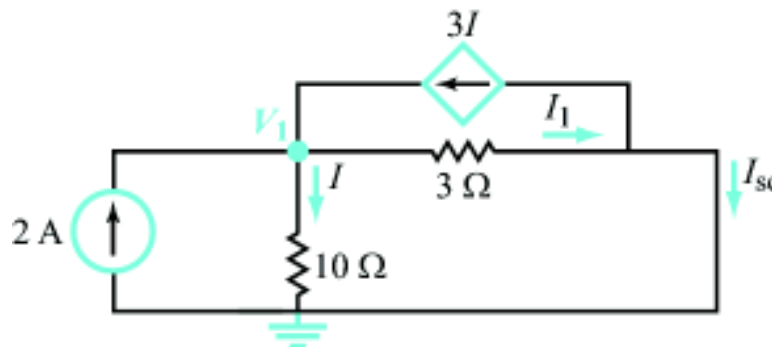Next, we determine the short-circuit current:



At node  $V_1$ :

$$-2 - 3I + \frac{V_1}{10} + \frac{V_1}{3} = 0.$$

Also,

$$I = \frac{V_1}{10}.$$

Hence,

$$-2 - 3I + I + \frac{10}{3}I = 0,$$

which gives

$$I = 1.5 \text{ A},$$

$$I_1 = 2 + 3I - I = 2 + 2I = 5 \text{ A},$$

$$I_{sc} = 5 - 3I = 5 - 4.5 = 0.5 \text{ A}.$$

$$R_{Th} = \frac{V_{Th}}{I_{sc}} = \frac{2}{0.5} = 4 \Omega.$$

Norton circuit is:

